
Assignment #01 - Turn on the Sequence! (TOS)

Schema breadboard:

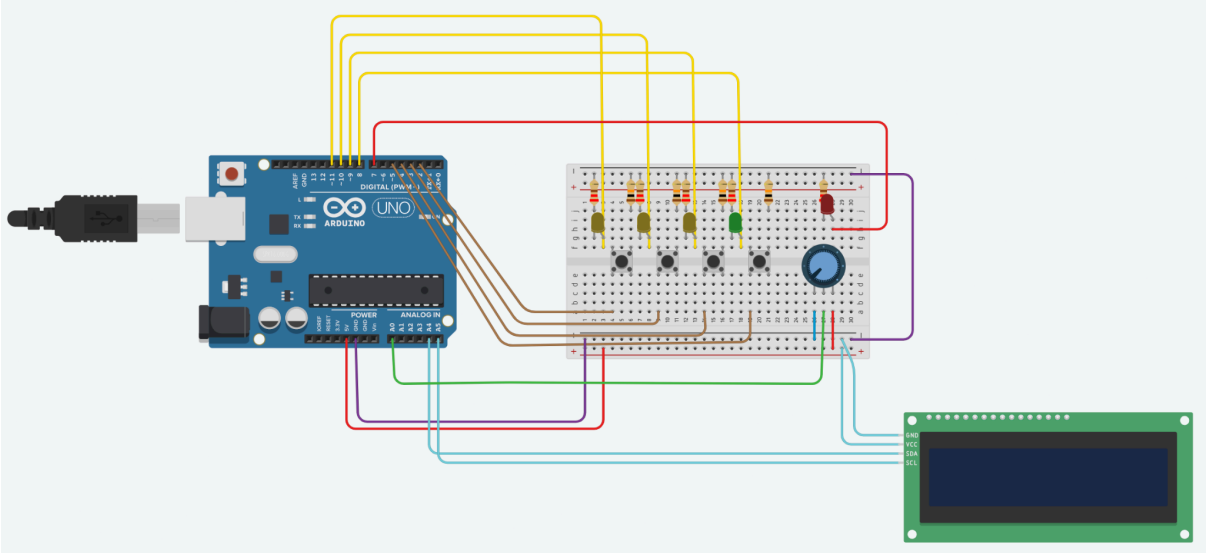

Link al video:
[assignment-01.mp4]